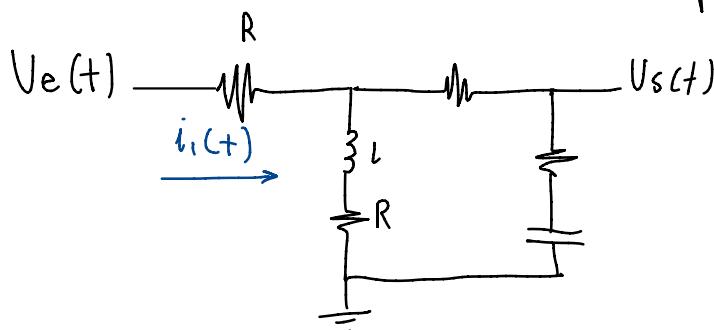


$$C = 100 \times 10^{-6}$$

$$L = 2.2 \times 10^{-3}$$

$$R = 1 \times 10^3 \Omega$$

13 - Sep - 25



Ecuaciones principales

$$2Ri_1(t)$$

$$Ri_1(t) - Ri_2(t)$$

$$U_e(t) = R i_1(t) + L \frac{d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)]$$

$$L \frac{d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)] = R i_2(t) + R i_2(t) + \frac{1}{C} \int i_2(t) dt$$

$$U_s(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt \quad 3R i_2(t)$$

despejar las dependientes de sdc donde no se int ni derive


$$i_1(t) = \left[U_e(t) - L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_2(t) \right] \frac{1}{2R}$$

$$i_2(t) = \left[L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_1(t) - \frac{1}{C} \int i_2(t) dt \right] \frac{1}{3R}$$

$$U_s(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt$$

Yodc10
ec
m1cgrc
d: ferentials

in
Voltage V_e .
go to from

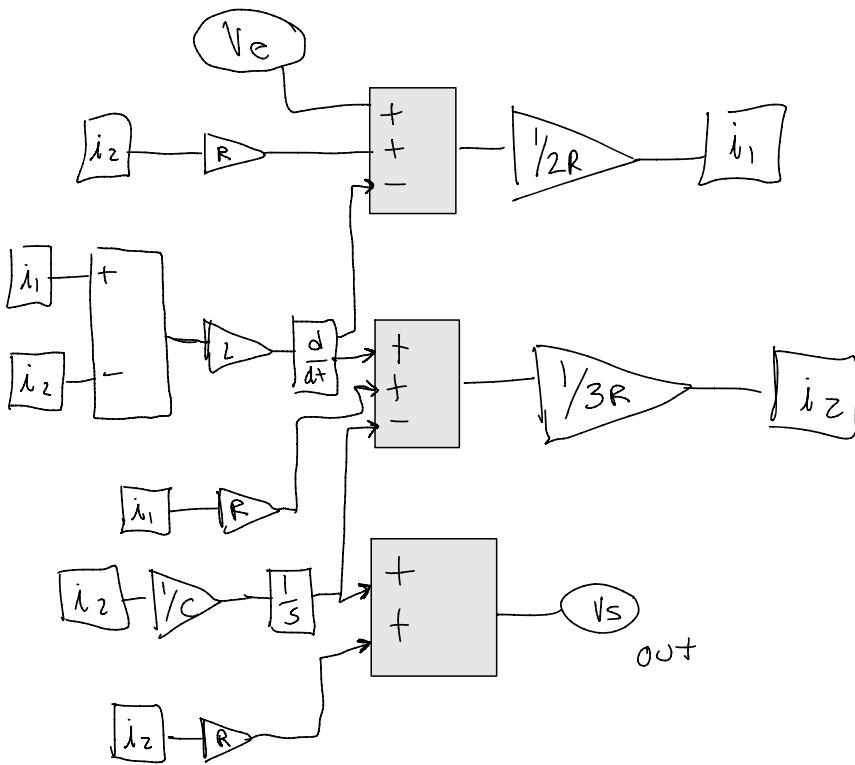

Con las ecuaciones principales continuaremos.

① Transformada de Laplace pasamos de dominio del t al dominio de s

$$V_e(s) = RI_1(s) + LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)]$$

$$2RI_1(s) + (LSI_1(s) - LSI_2(s)) - RI_2(s)$$

$$= (2R + LS)I_1(s) - (LS + R)I_2(s)$$

②

$$LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)] = 2RI_2(s) + \frac{I_2(s)}{Cs}$$

$$L\bar{S}I_1(s) - L\bar{S}I_2(s) + R\bar{I}_1(s) - R\bar{I}_2(s) = 2R\bar{I}_2(s) + \frac{\bar{I}_2(s)}{Cs}$$

$$L\bar{S}I_1(s) + R\bar{I}_1(s) = L\bar{S}I_2(s) + 3R\bar{I}_2(s) + \frac{\bar{I}_2(s)}{Cs}$$

$$(Ls + R)\bar{I}_1(s) = (Ls + 3R + \frac{1}{Cs})\bar{I}_2(s)$$

$$\bar{I}_1(s) = \frac{CLS^2 + 3CRS + 1}{Cs(Ls + R)} \bar{I}_2(s)$$

Ahora el V_s

$$V_s(s) = \left(R + \frac{1}{Cs} \right) \bar{I}_2(s)$$

$$= \frac{CRS + 1}{Cs} \bar{I}_2(s)$$

Termina la parte y empieza el algebraico

$$V_e(s) = (2R + LS) \left(\frac{CLS^2 + 3CRS + 1}{Cs(Ls + R)} \right) \bar{I}_2(s) - (2s + R) \bar{I}_2(s)$$

$$V_e(s) = \left[\frac{(2R + LS)(CLS^2 + 3CRS + 1)}{Cs(Ls + R)} - (LS + R) \right] \bar{I}_2(s)$$

$$= \left[\frac{(2R + LS)(CLS^2 + 3CRS + 1) - Cs(Ls + R)(LS + R)}{Cs(Ls + R)} \right]$$

~~$$= 2CLR S^2 + 6CR^2 S + 2R + CL^2 S^3 + 3CLRS^2 + CS$$~~
~~$$- CL^2 S^3 - CLR S^2 - CLRS^2 - CR^2 S$$~~

$$\frac{CS(Ls + R)}{I_2(s)}$$

$$\frac{V_c(s) = 3CLR s^2 + (5CR^2 + L)s + 2R}{CS(2s + R)} \quad I_2(s)$$

$$\frac{V_s(s)}{V_c(s)} = \frac{\frac{CRs+1}{Cs} I_2(s)}{\frac{3CLRs^2 + (5CR^2 + L)s + 2R}{Cs(2s + R)} I_2(s)}$$

$$= \frac{(CRs+1)(2s+R)}{3CLRs^2 + (5CR^2 + L)s + 2R} = \frac{CLRs^2 + (CR^2 + L)s + R}{3CLRs^2 + (5CR^2 + L)s + 2R}$$


$$e(t) = \frac{R}{2R} = \frac{1}{2}$$

Con nuestros valores de R (L

Error en estado estacionario [escalón unitario]

$$\begin{aligned} e(s) &= \lim_{s \rightarrow 0} s V_e(s) \left[1 - \frac{V_s(s)}{V_e(s)} \right] \\ &= \lim_{s \rightarrow 0} s * \frac{1}{s} \left[1 - \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R} \right] \\ &= \frac{R}{2R} \\ &= \frac{1}{2} v \end{aligned}$$

Bosquejo ↗

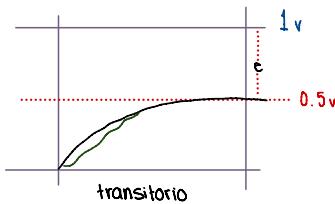

Estabilidad en lazo abierto

- Cálculo de raíces del denominador [Polos]

$$3CLRS^2 + (5CR^2 + L)s + 2R = 0$$

Con base en las raíces, se concluye que el sistema es estable con una respuesta Sobreacortiguada.

$$\text{den} = [3 * C * L * R, 5 * C * R ** 2 + L, 2 * R]$$

$$\lambda_1 = -4.464285713 \times 10^7$$

$$\lambda_2 = -7.843137257 \times 10^{-2}$$

$$\lambda_1 = -7.57575091 \times 10^5$$

$$\lambda_2 = -4.00000352$$